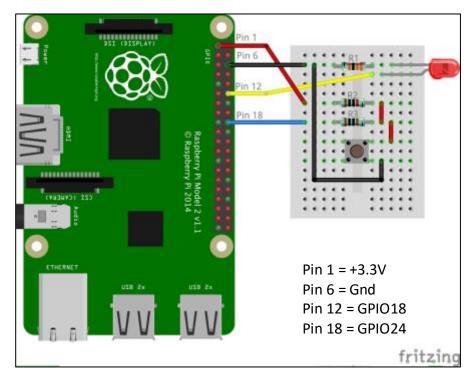
SCRATCH 1.4 - GPIO Exercise - Switching LED



Components:

R1 – Resistor 330 ohms

R2 - Resistor 10K ohms

R3 - Resistor 1K ohms

LED

Switch

Breadboard

Connecting wires

Assemble the components:

Ensure the LED is connected the correct way, long pin + to Pin 12.

Test the circuit: Use a spare connector

1. Connect between left hand side of R2 and the long lead of the LED. The LED should light. Remove connector; the test is complete.

Coding – Open SCRATCH 1.4 on the Raspberry Pi

2. Open the Edit menu and start the GPIO Server

3. The code blocks used for controlling the GPIO are all actioned using the Control broadcast block. For example to turn on the GPIO server:	broadcast gpioserveron ▼
4. To select and switch on a GPIO output: read the caption as: configure GPIO 18 as an output gpio18 switch on [Options: on, high, off, low]	broadcast config18out ▼ broadcast gpio18on ▼
5. Bring it all together as a script. Run this code and the LED should come on Challenge: How do you switch the LED off? Try it!	when clicked broadcast gpioserveron broadcast config18out broadcast gpio18on
6. Accept a command from a switch to activate the LED. Add the following block:	broadcast config24inpullup ▼

